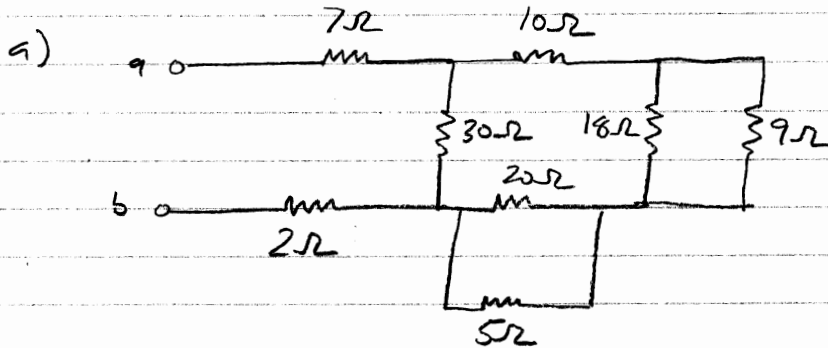


Problem Set 2 (Chapt 2)

① P22




Note: $// \rightarrow$ parallel

⊙ Determine equivalent resistance R_{eq} between a+b.

$$\bullet 18\Omega // 9\Omega = \frac{1}{\frac{1}{18\Omega} + \frac{1}{9\Omega}} = \frac{1}{\frac{3}{18\Omega}} = 6\Omega$$


$$\bullet 20\Omega // 5\Omega = \frac{1}{\frac{1}{20\Omega} + \frac{1}{5\Omega}} = \frac{1}{\frac{5}{20\Omega}} = 4\Omega$$

We can redraw circuit as

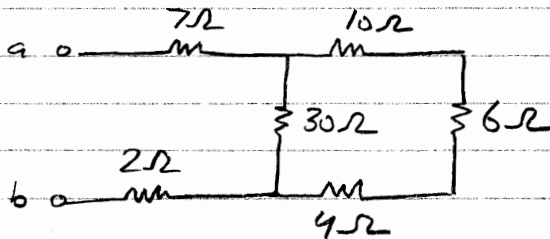


$$\bullet 10\Omega + 6\Omega + 4\Omega = 20\Omega$$



We can redraw circuit as

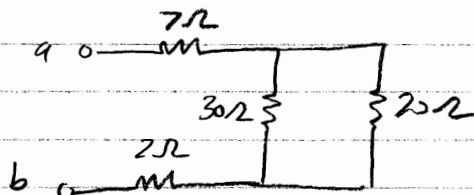
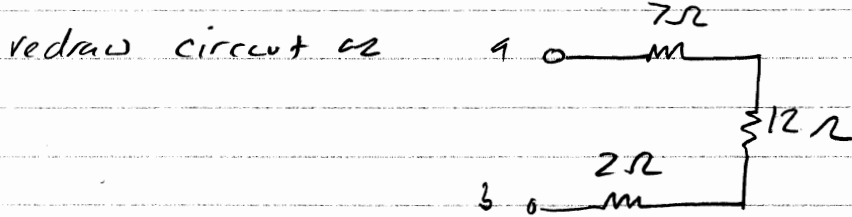
$$\bullet 30 // 20\Omega = \frac{1}{\frac{1}{30\Omega} + \frac{1}{20\Omega}} = \frac{1}{\frac{5}{60\Omega}} = 12\Omega$$



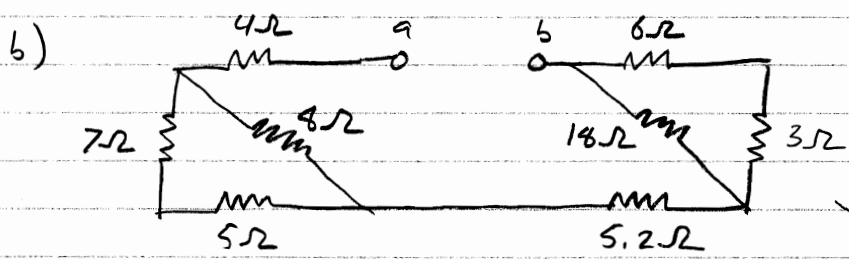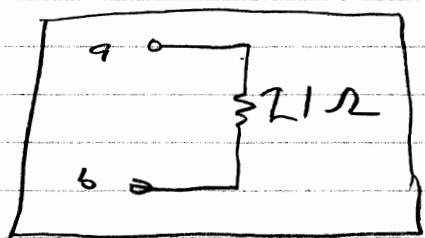• $7\Omega + 12\Omega + 2\Omega = \underline{\underline{21\Omega}}$



this side reduces to:

$$4\Omega + \left[\frac{1}{\frac{1}{12\Omega} + \frac{1}{8\Omega}} \right]$$

$$= 4\Omega + \left[\frac{1}{\frac{1}{12\Omega} + \frac{1}{8\Omega}} \right]$$

$$= 4\Omega + \frac{24}{5}\Omega = \underline{\underline{\frac{44}{5}\Omega}}$$

this side reduces to:


$$\left(18\Omega \parallel (6\Omega + 3\Omega) \right) + 5.2\Omega$$

$$\left(\frac{1}{\frac{1}{18\Omega} + \frac{1}{9\Omega}} \right) + 5.2\Omega$$


$$6\Omega + 5.2\Omega$$

$$= \underline{\underline{11.2\Omega}}$$

We can redraw the circuit as.

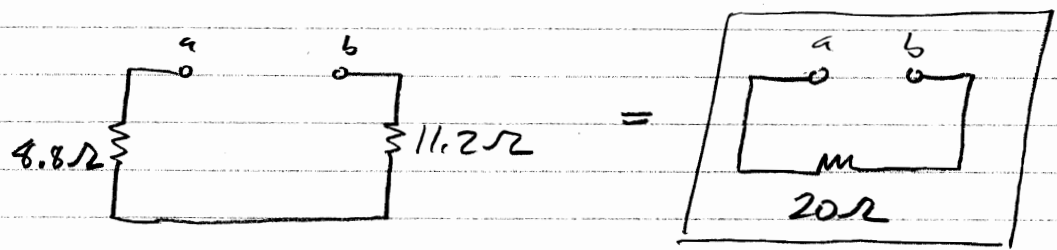

2. P2.22 Find the values of i_1 & i_2

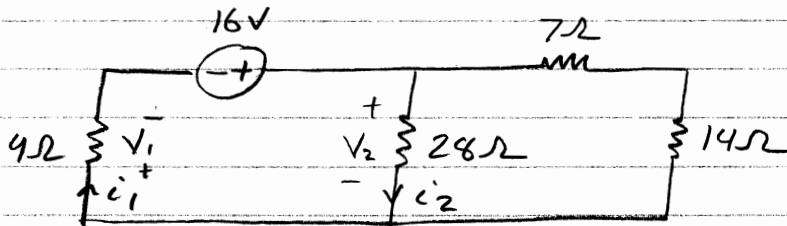


First will find i_1 by drawing equivalent circuit.

$$R_{eq} = [28\Omega \parallel (7\Omega + 14\Omega)] + 4\Omega$$

$$= \frac{1}{\frac{1}{28\Omega} + \frac{1}{21\Omega}} + 4\Omega$$

$$= 12 + 4\Omega = 16\Omega$$

So equivalent circuit is

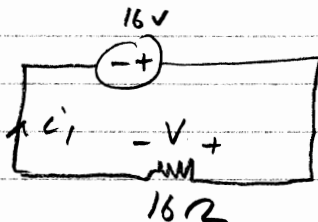

$$\text{KVL: } -16V + V = 0$$

$$V = 16V$$

$$\text{Ohm's: } i_1 = \frac{V}{R} = \frac{16V}{16\Omega} = 1\text{Amp.}$$


To get i_2 , write KVL equation round inner loop.

$$-16V + V_2 + V_1 = 0$$

$$-16V + i_2(28\Omega) + (1A)(4\Omega) = 0$$

$$i_2 = \frac{16V - 4V}{28\Omega} = 0.43\text{Amps}$$

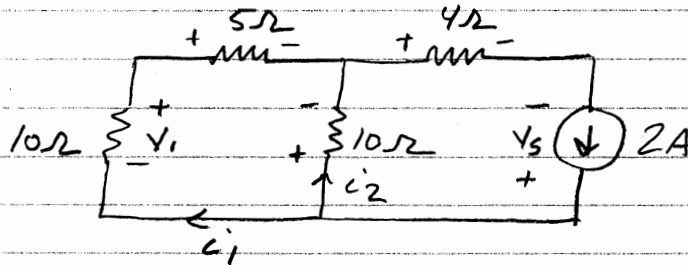3. P 2.23 Find the values of V_s , V_1 , + i_2




First, will get V_s by combining R 's into equivalent resistance.

$$R_{eq} = 4\Omega + [10\Omega \parallel (10\Omega + 5\Omega)]$$

$$= 4\Omega + \left[\frac{1}{\frac{1}{10\Omega} + \frac{1}{15\Omega}} \right]$$

$$= 4\Omega + 6\Omega = \underline{\underline{10\Omega}}$$

\therefore Equivalent circuit is

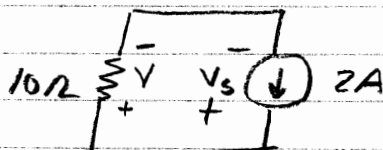

$$\text{KVL: } -V_s + V = 0$$

$$V_s = V = (2A)(10\Omega) = 20V \quad \checkmark$$

Now can find i_1 + i_2 by writing KVL equations around loops of original circuit.

$$-V_s + (10\Omega)(i_2) + (4\Omega)(2A) = 0$$

$$i_2 = \frac{V_s - 8V}{10\Omega} = \frac{20V - 8V}{10\Omega} = 1.2 \text{ Amps} \quad \checkmark$$

likewise:

$$-V_s - V_1 + (5\Omega)(i_1) + (4\Omega)(2A) = 0$$

$$V_1 = \underline{8V - V_s + (5\Omega)(i_1)}$$

What is i_1 ?


$$\text{KCL: } i_1 + i_2 = 2A$$

$$i_1 = 2A - i_2 = 2A - 1.2A = 0.8A. \checkmark$$

$$\therefore V_1 = 8V - 20V + (5\Omega)(0.8A)$$

$$\boxed{V_1 = -8V} \checkmark$$

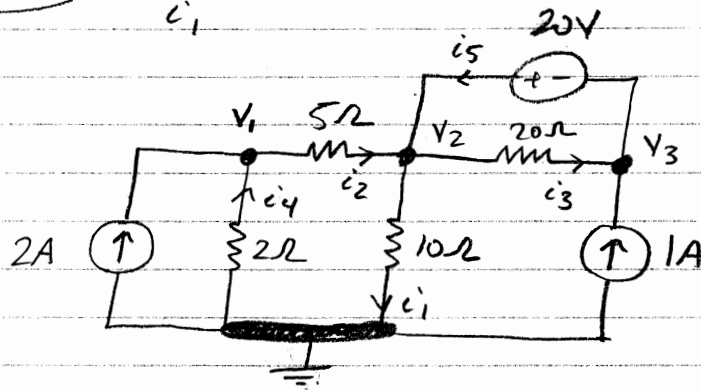4. P2.43 Use node-voltage technique to find i_1



1. ID nodes.
2. Assign currents
3. Assign voltages and choose ground.
4. Obvious relations:

$$V_2 - V_3 = 20V$$

5. Apply KCL

$$\begin{aligned} V_1: & 2A + i_4 = i_2 \\ V_2: & i_2 + i_5 = i_1 + i_3 \\ V_3: & i_3 + 1A = i_5 \\ \text{ground:} & 2A + 1A + i_4 = i_1 \end{aligned} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \begin{array}{l} \text{supernode: } i_1 + i_3 - i_2 = i_3 + 1A \\ i_1 - i_2 = 1A \end{array}$$

6. Write i 's in terms of V 's

$$\begin{aligned} V_1: & 2A + \frac{0 - V_1}{2\Omega} = \frac{V_1 - V_2}{5\Omega} \\ \text{Supernode:} & \frac{V_2 - 0}{10\Omega} - \frac{V_1 - V_2}{5\Omega} = 1A \\ \text{ground:} & 3A + \frac{0 - V_1}{2\Omega} = \frac{V_2 - 0}{10\Omega} \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \begin{array}{l} \text{Have 3 eqns and} \\ \text{2 unknowns} \\ \text{Solvable } \checkmark \end{array}$$

7. Solve system:

$$V_1 = (2A)(10\Omega) - 5V_1 = 2(V_1 - V_2)$$

$$\underline{20V - 7V_1 + 2V_2 = 0} \quad \checkmark$$

Super node:

$$V_2 - 2V_1 + 2V_2 = 10V$$

$$V_2 = \frac{10V + 2V_1}{3} \quad \checkmark \leftarrow \text{Sub into } V_1 \text{ eqn.}$$

$$20V - 7V_1 + 2\left(\frac{10V + 2V_1}{3}\right) = 0$$


$$V_1 = 4.7V \quad !$$

$$\underline{V_2 = 6.5V} \quad !$$

8. Use V_2 to solve for i_1

$$i_1 = \frac{V_2 - 0}{10\Omega} = \frac{6.5V}{10\Omega} = \boxed{0.65A} \quad \checkmark$$

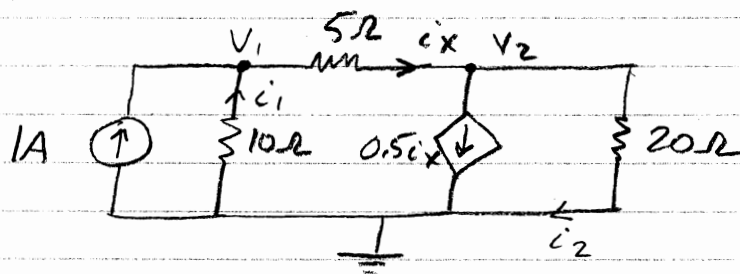5. P2.46. Solve for values of node voltages V_1 & V_2 , then solve for i_x .



1. ID nodes
2. Assign currents
3. Assign voltages
4. Notice obvious relations - none that I can see
5. KCL

$$V_1: 1A + i_1 = i_x$$

$$V_2: i_x = 0.5i_x + i_2$$

$$0.5i_x = i_2$$

$$\text{ground: } i_2 + 0.5i_x = i_1 + 1A$$

6. Write i's in terms of V's

$$V_1: 1A + \frac{0 - V_1}{10\Omega} = \frac{V_1 - V_2}{5\Omega}$$

$$V_2: \frac{0.5(V_1 - V_2)}{5\Omega} = \frac{V_2 - 0}{20\Omega}$$

$$\text{ground: } \frac{V_2 - 0}{20\Omega} + 0.5 \frac{(V_1 - V_2)}{5\Omega} = \frac{0 - V_1}{10\Omega} + 1A$$

7. solve system:

$$V_1: (10\Omega)(1A) - V_1 = 2V_1 - 2V_2$$

$$\underline{10V - 3V_1 + 2V_2 = 0}$$

$$V_2: \quad 2V_1 - 2V_2 = V_2$$
$$\underline{2V_1 = 3V_2}$$

$$\therefore V_2 = \frac{2}{3}V_1 \leftarrow \text{plug into eq for } V_1$$

$$10V - 3V_1 + 2\left(\frac{2}{3}V_1\right) = 0$$

$$10V - 1.67V_1 = 0$$

$$\boxed{V_1 = 6.01V}$$


$$V_2 = \frac{2}{3}(6V) = \boxed{4V}$$

6. Solve for i_x

$$i_x = \frac{V_1 - V_2}{5\Omega} = \frac{6V - 4V}{5\Omega} = \boxed{0.4 \text{ Amp.}} \checkmark$$

P2.48

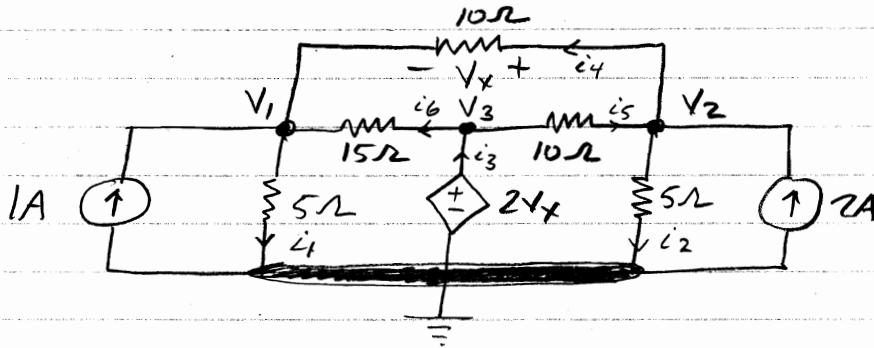⑥ Solve for node voltages V_1 + V_2 , then find V_x .



1. 1D nodes
2. Assign currents
3. Assign voltages to nodes
4. obvious relations:

$$V_3 - 0 = 2V_x \quad \underline{V_x = V_2 - V_1}$$

$$\underline{V_3 = 2V_x}$$

5. Apply KCL

$$V_1: \underline{1A + i_6 + i_4 = i_1}$$

$$V_2: \underline{2A + i_5 = i_2 + i_4}$$

$$V_3: i_3 = i_6 + i_5$$

$$\text{ground: } 1A + 2A + i_3 = i_1 + i_2$$

} Super node:

$$\underline{i_6 + i_5 = i_1 + i_2 - 3A}$$

6. i 's \rightarrow V 's

$$V_1: 1A + \frac{V_3 - V_1}{15\Omega} + \frac{V_2 - V_1}{10\Omega} = \frac{V_1}{5\Omega}$$

$$30V + 2V_3 - 2V_1 + 3V_2 - 3V_1 = 6V_1$$

$$\underline{30V - 11V_1 + 3V_2 + 2V_3 = 0}$$

$$V_2: \quad 2A + \frac{V_3 - V_2}{10\Omega} = \frac{V_2}{5\Omega} + \frac{V_2 - V_1}{10\Omega}$$

$$20V + V_3 - V_2 = 2V_2 + V_2 - V_1$$

$$\underline{20V + V_1 - 4V_2 + V_3 = 0}$$

Supernode: note: the supernode current equation is a superposition of V_1 & V_2 equations, therefore does not provide additional information.

Other equations we can use are: $V_3 = 2V_2$ & $V_2 = V_2 - V_1$

$$\therefore \underline{V_3 = 2V_2 - 2V_1}$$

7. Solve system:

$$V_3 = 2V_2 - 2V_1$$

plug into other two eqns:

$$\bullet \quad 20V + V_1 - 4V_2 + 2V_2 - 2V_1 = 0$$

$$\underline{20V - V_1 - 2V_2 = 0}$$

$$\bullet \quad 30V - 11V_1 + 3V_2 + 2(2V_2 - 2V_1) = 0$$

$$\underline{30V - 15V_1 + 7V_2 = 0}$$

$$\begin{aligned} & -15(20V - V_1 - 2V_2) = 0 \\ + & \quad 30V - 15V_1 + 7V_2 = 0 \\ & \underline{-270V + 37V_2 = 0} \end{aligned}$$


$$\boxed{\therefore V_2 = 7.3V} \quad \checkmark$$

now solve for V_1

$$V_1 = \frac{7(V_2) + 30V}{15} = \frac{7(7.3) + 30V}{15}$$

$$V_1 = 5.4V \quad \checkmark$$

7 P 2.53

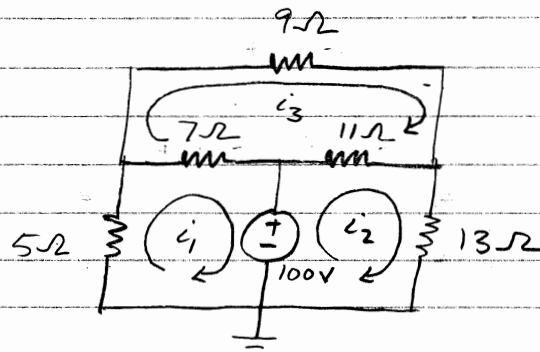

Solve for mesh currents shown (i_1 , i_2 , i_3)

1. 1D loops
2. Assign currents
3. Obvious relations: none
4. Apply KVL

$$i_1: 100V + V_{5\Omega} + V_{7\Omega} = 0$$

$$i_2: -100V + V_{11\Omega} + V_{13\Omega} = 0$$

$$i_3: V_{9\Omega} + V_{11\Omega} + V_{7\Omega} = 0$$

5. $V_i \rightarrow i$'s

$$i_1: 100V + i_1 5\Omega + (i_1 - i_3) 7\Omega = 0$$
$$100V + i_1 12\Omega - i_3 7\Omega = 0$$

$$i_2: -100V + (i_2 - i_3) 11\Omega + i_2 13\Omega = 0$$
$$-100V + i_2 (24\Omega) - i_3 11\Omega = 0$$

$$i_3: i_3 9\Omega + (i_3 - i_2) 11\Omega + (i_3 - i_1) 7\Omega = 0$$
$$i_3 27\Omega - i_2 11\Omega - i_1 7\Omega = 0$$

6. Solve system

- from i_1 : $i_1 = \frac{i_3 7\Omega - 100V}{12\Omega}$

$$\underline{i_1 = \frac{7}{12} i_3 - 8.33A}$$

- plug into eq for i_3 :

$$i_3 27\Omega = i_2 11\Omega - 7\Omega \left(\frac{7}{12} i_3 - 8.33A \right) = 0$$

$$-i_3 27\Omega - i_2 11\Omega - 4.1\Omega i_3 + 58.3V = 0$$

$$i_3 22.9\Omega = i_2 11\Omega - 58.3V$$

$$i_2 = \frac{i_3 22.9\Omega + 58.3V}{11\Omega} = 2.08 i_3 + 5.3A$$

- plug into eq for i_2 :

$$-100V + (2.08 i_3 + 5.3A) 24\Omega - i_3 11\Omega = 0$$


$$-100V + 49.9 i_3 + 127.2V - i_3 11\Omega = 0$$

$$\boxed{i_3 = -0.7A} \quad \checkmark$$

$$i_2 = 5.3A + 2.08(-0.7A) = \boxed{3.8A} \quad \checkmark$$

$$i_1 = \frac{7}{12} (-0.7A) - 8.33A = \boxed{-8.7A} \quad \checkmark$$

⑧ P2.60

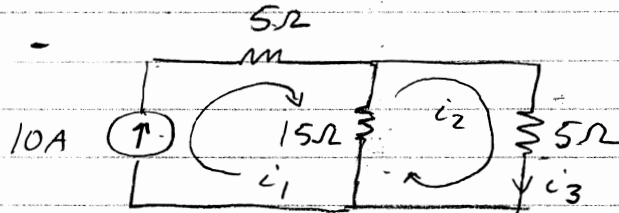

Use Mesh analysis to obtain i_3

1. 1D loops
2. Assign currents
3. Obvious relations: $i_2 = i_3$, $i_1 = 10A$
4. KVL.

i_1 : not a good one

$$i_2: V_{5\Omega} + V_{15\Omega} = 0$$

5. $V_s \rightarrow i_s$

i_1 : not a good one

$$i_2 = i_2 5\Omega + (i_2 - i_1) 15\Omega = 0$$


$$\underline{i_2 20\Omega - i_1 15\Omega = 0}$$

6. solve system

$$i_2 20\Omega - (10A) 15\Omega = 0$$

$$i_2 = \boxed{7.5 \text{ Amps} = i_3} \quad \checkmark$$

9. P2.62 Use mesh analysis to find V_3

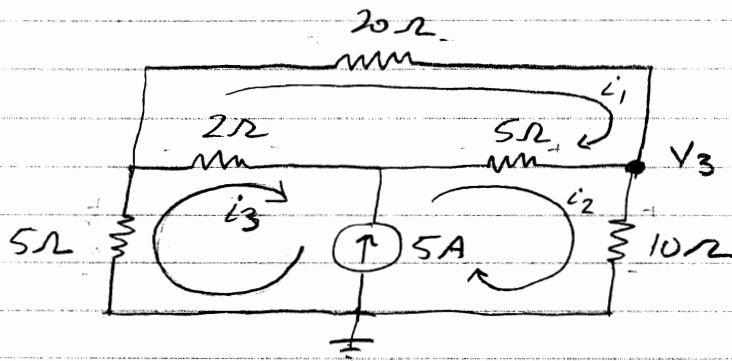

1. 10 loops

2. Assign currents

3. obvious relations

$$\underline{i_2 - i_3 = 5A} \quad \textcircled{1}$$

4. KVL:

$$i_1: V_{20\Omega} + V_{5\Omega} + V_{2\Omega} = 0$$

i_2 : not a good one

i_3 : not a good one

5. $V_3 \rightarrow i_3$

$$i_1: i_1 20\Omega + (i_1 - i_2) 5\Omega + (i_1 - i_3) 2\Omega = 0$$

$$\underline{i_1 27\Omega - i_2 5\Omega - i_3 2\Omega = 0} \quad \textcircled{2}$$

note: we have 3 unknowns but only two eqns.
- need one more.

Write KVL eqn around loop containing both i_3 & i_2

$$\underline{i_2 10\Omega + i_3 5\Omega + (i_3 - i_1) 2\Omega + (i_2 - i_1) 5\Omega = 0}$$

$$\underline{-i_1 7\Omega + i_2 15\Omega + i_3 7\Omega = 0} \quad \textcircled{3}$$

6. Solve system

from ① get $i_2 = 5A + i_3$

- plug this into eq ② + ③

$$i_1 27\Omega - (5A + i_3) 5\Omega - i_3 2\Omega = 0$$

$$i_1 27\Omega - i_3 7\Omega - 25V = 0$$

- $-i_1 7\Omega + (5A + i_3) 5\Omega + i_3 7\Omega = 0$

$$-i_1 7\Omega + i_3 22\Omega + 75V = 0$$

$$i_1 = \frac{+75V + i_3 22\Omega}{7\Omega}$$

- $\left(\frac{75V + i_3 22\Omega}{7\Omega} \right) 27\Omega - i_3 7\Omega - 25V = 0$

$$289.3V + 84.9\Omega i_3 + i_3 7\Omega - 25V = 0$$

$$i_3 = \frac{-264.3V}{91.9\Omega} = -3.4 \text{ Amps}$$

7. Use i_3 to get i_2 and V_3

$$i_2 = 5A + i_3 = 5A - 3.4 \text{ Amps} = 1.6 \text{ Amps}$$

$$V_3 - 0 = i_2 10\Omega = (1.6A) 10\Omega = \boxed{-16V}$$